

香 港 中 文 大 學
The Chinese University of Hong Kong
二零二二至二三年度上學期科目考試
Course Examination 1st Term, 2022-23

科目編號及名稱
Course Code & Title : **IERG 2060 Basic Analog and Digital Circuits**


時間
Time allowed : 2 小時 0 分鐘
hours minutes

學號
Student I.D. No. : 座號
Seat No. :

- This paper comprises **EIGHT** questions.
- Answer **ANY FOUR** questions from Questions 1 to 5 **AND** answer **ALL** from Questions 6 to 8.
- Each question carries **20 points**
- Total score of this paper is **140 points**.


Question 1

In the following circuit, determine the maximum power transferred to the resistor R .

 **Question 2**

In the following circuit,


- (a) determine the current i_x , and voltage v_o .
- (b) determine the power dissipated by the $60\text{k}\Omega$ resistor.

  


Question 3

In the following circuit, initially, both switches S_1 and S_2 are opened for a long time. Switch S_1 is closed at $t=0$, while switch S_2 is closed at $t=4$. Determine the current i passing through the inductor,

- (a) for $t > 0$ (and before switch S_2 is closed), and
- (b) for $t > 4$, (after switch S_2 is closed)

**Question 4**

 In the following circuit, the switch is closed at $t=0$. Find i_x for $t > 0$, assuming $R_1=R_2=2\text{k}\Omega$, $R_3=4\text{k}\Omega$, and $C=0.25\text{mF}$.

 


Question 5


In the following AC circuit, using phasor method,

- determine the Thévenin equivalent impedance across ports $a-b$.
- determine the Thévenin equivalent voltage across ports $a-b$.

*Express your answers in rationalized complex number form, that is, $x+jy$.

 **Question 6**

- The following figure shows a logic gate circuit using CMOS gates. Write a truth table with two inputs, A and B , and output Y . Determine the name of this logic function.




- For each of the following Boolean expressions, **simplify** the expression and **sketch** the simple combinational circuit to realize your answer. Label the inputs and output clearly.

(i) $Y = ABCD + \bar{A}B\bar{C}D + (\bar{B} + D)E$

(ii) $Y = \bar{A}\bar{B} + \bar{A}B\bar{C} + (\bar{A} + C)$

 Question 7

Consider the following logic circuit with one J-K flip-flop and one D flip-flop. x is the input variable and z is the output variable. Clock is the clock input.



- Express the boolean expressions for the inputs of the J-K flip-flop and the D flip-flop, namely J , K , and D , in terms of the input variable x , and their current state variables, q_1 , q_1' , q_2 and q_2' .
- Express the boolean expression for the output variable z , in terms of the input variable x , and their current state variables, q_1 , q_1' , q_2 and q_2' .
- Write down the state transition table, in terms of present states, input, next states, output and the flip-flop inputs.
- Construct the state diagram, labelled with states in circles, and input/output on each arrow.

Question 8

Design a synchronous counter that goes through the following sequence:

$1 \rightarrow 3 \rightarrow 5 \rightarrow 7 \rightarrow 4 \rightarrow 2 \rightarrow 0 \rightarrow 6 \rightarrow$ and repeat

using D flip flops. Please perform the following procedures:

- define the input variables,
- determine the required number of flip flops,
- show a state-transition table,
- derive the Boolean expressions for the inputs of the flip flops and output, and
- construct a labelled logic circuit diagram.

**** END ****

APPENDIX

Axiom		Dual		Name
A1	$B = 0 \text{ if } B \neq 1$	A1'	$B = 1 \text{ if } B \neq 0$	Binary field
A2	$\overline{0} = 1$	A2'	$\overline{1} = 0$	NOT
A3	$0 \bullet 0 = 0$	A3'	$1 + 1 = 1$	AND/OR
A4	$1 \bullet 1 = 1$	A4'	$0 + 0 = 0$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	A5'	$1 + 0 = 0 + 1 = 1$	AND/OR

Theorem		Dual		Name
T1	$B \bullet 1 = B$	T1'	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	T2'	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	T3'	$B + B = B$	Idempotency
T4		$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	T5'	$B + \overline{B} = 1$	Complements

Theorem		Dual		Name
T6	$B \bullet C = C \bullet B$	T6'	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	T7'	$(B + C) + D = B + (C + D)$	Associativity
T8	$(B \bullet C) + B \bullet D = B \bullet (C + D)$	T8'	$(B + C) \bullet (B + D) = B + (C \bullet D)$	Distributivity
T9	$B \bullet (B + C) = B$	T9'	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \overline{C}) = B$	T10'	$(B + C) \bullet (B + \overline{C}) = B$	Combining
T11	$(B \bullet C) + (\overline{B} \bullet D) + (C \bullet D)$ $= B \bullet C + \overline{B} \bullet D$	T11'	$(B + C) \bullet (\overline{B} + D) \bullet (C + D)$ $= (B + C) \bullet (\overline{B} + D)$	Consensus
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots}$ $= (\overline{B_0} + \overline{B_1} + \overline{B_2} \dots)$	T12'	$\overline{B_0 + B_1 + B_2 \dots}$ $= (\overline{B_0} \bullet \overline{B_1} \bullet \overline{B_2})$	De Morgan's Theorem

De Morgan's Theorem $\overline{A \bullet B} = \overline{A} + \overline{B}$; $\overline{A + B} = \overline{A} \bullet \overline{B}$


(a) JK Flip-Flop				(b) SR Flip-Flop			
J	K	$Q(t+1)$	Operation	S	R	$Q(t+1)$	Operation
0	0	$Q(t)$	No change	0	0	$Q(t)$	No change
0	1	0	Reset	0	1	0	Reset
1	0	1	Set	1	0	1	Set
1	1	$\overline{Q}(t)$	Complement	1	1	?	Undefined

(c) D Flip-Flop			(d) T Flip-Flop		
D	$Q(t+1)$	Operation	T	$Q(t+1)$	Operation
0	0	Reset	0	$Q(t)$	No change
1	1	Set	1	$\overline{Q}(t)$	Complement






J-K flip flop: $Q^+ = J \cdot \overline{Q} + \overline{K} \cdot Q$

T flip flop: $Q^+ = T \cdot \overline{Q} + \overline{T} \cdot Q$

CMOS Logic

 

Summary of basic op amp circuits.

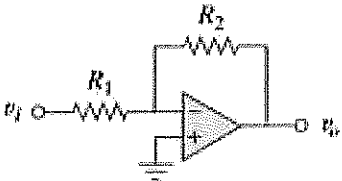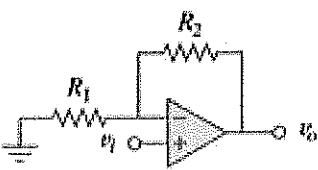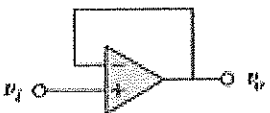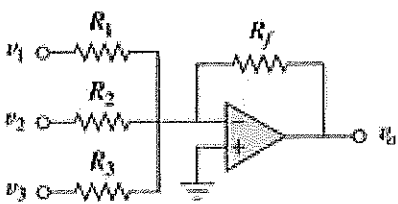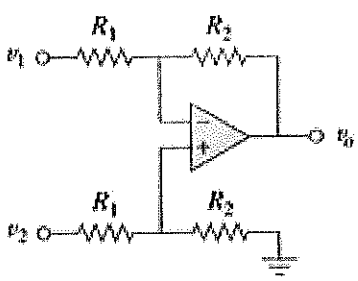Op amp circuit	Name/output-input relationship
	Inverting amplifier $v_o = -\frac{R_2}{R_1}v_i$
	Noninverting amplifier $v_o = \left(1 + \frac{R_2}{R_1}\right)v_i$
	Voltage follower $v_o = v_i$
	Summer $v_o = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2 + \frac{R_f}{R_3}v_3\right)$
	Difference amplifier $v_o = \frac{R_2}{R_1}(v_2 - v_1)$